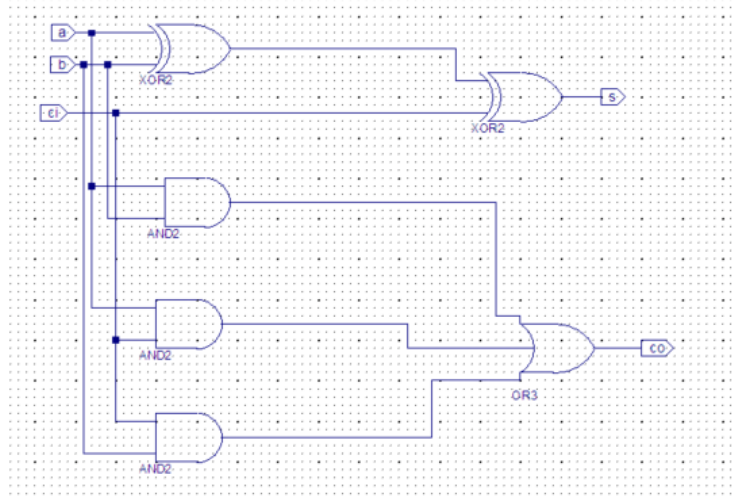



EE533 Lab2

1. Designing and Simulating Synchronous 8-bit adder


1-bit adder schematic:



8-bits adder schematic:

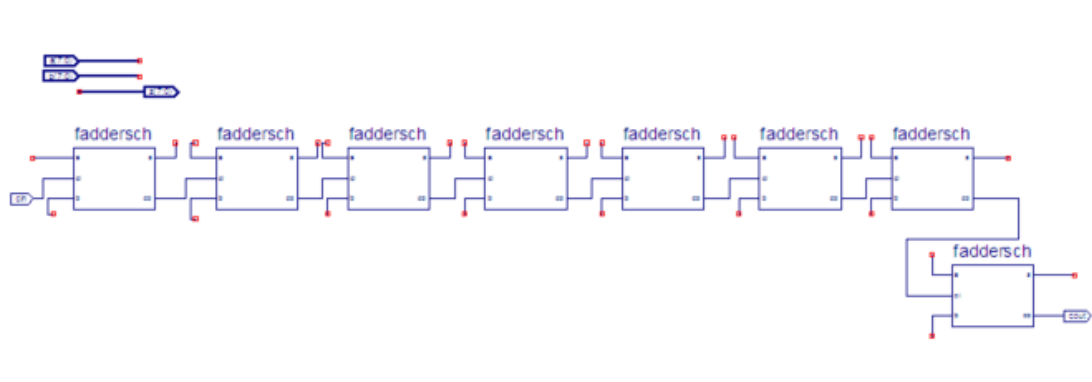


8-bits adder testbench:

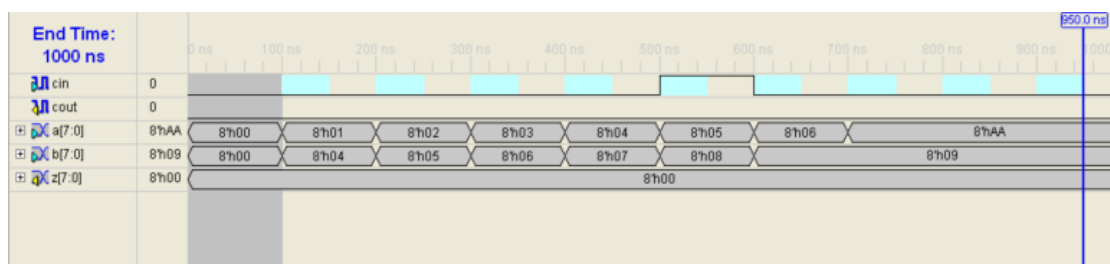

Current Simulation Time: 1000 ns		300 ns	350 ns	400 ns	450 ns	500 ns	550 ns	600 ns	650 ns	700 ns	750 ns	800 ns	850 ns	900 ns	950 ns	1000 ns
cout	0															
cIn	0															
a[7:0]	8'hAA	8'h03		8'h04		8'h05		8'h06					8'hAA			
b[7:0]	8'h09	8'h06		8'h07		8'h08						8'h09				
z[7:0]	8'hB3	8'h09		8'h0B		8'h0E		8'h0F					8'hB3			

Schematic:

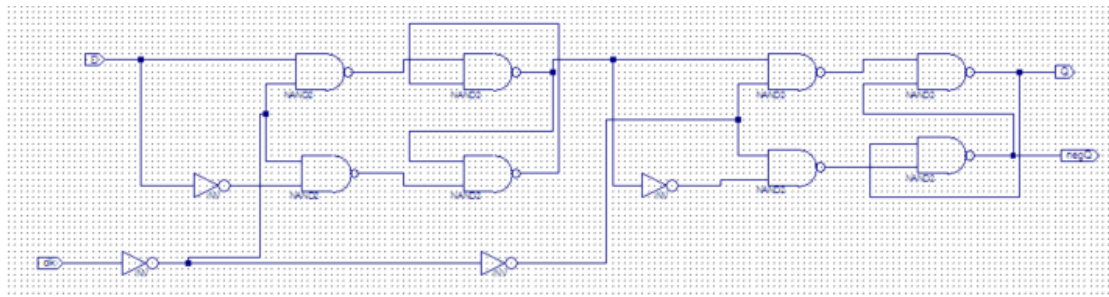


Timing diagram showing signals clk, D, Q, and negQ over 1000 ns. The signals are as follows:

Signal	Value
clk	0
D	1
Q	0
negQ	0


Current Simulation Time: 1000 ns		0 ns	100 ns	200 ns	300 ns	400 ns	500 ns	600 ns	700 ns	800 ns	900 ns	1000 ns	
clk	1												
D	1												
Q	1												
negQ	0												

8bit fulladder with dff


Schematic:

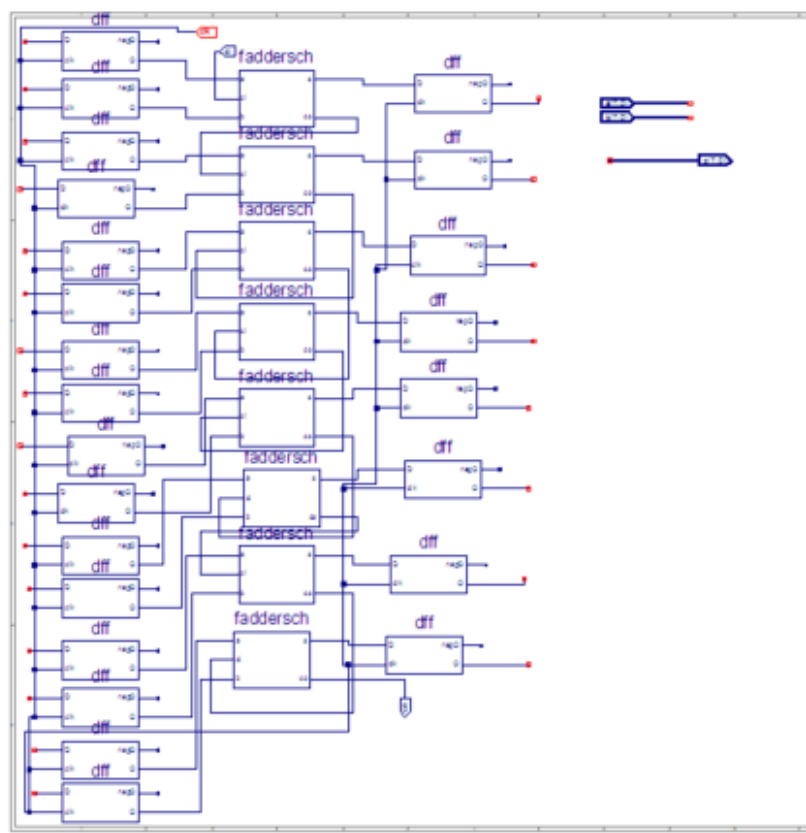

Testbench:

 


Simulation result:

 


32bit fulladder with dff


Schematic:

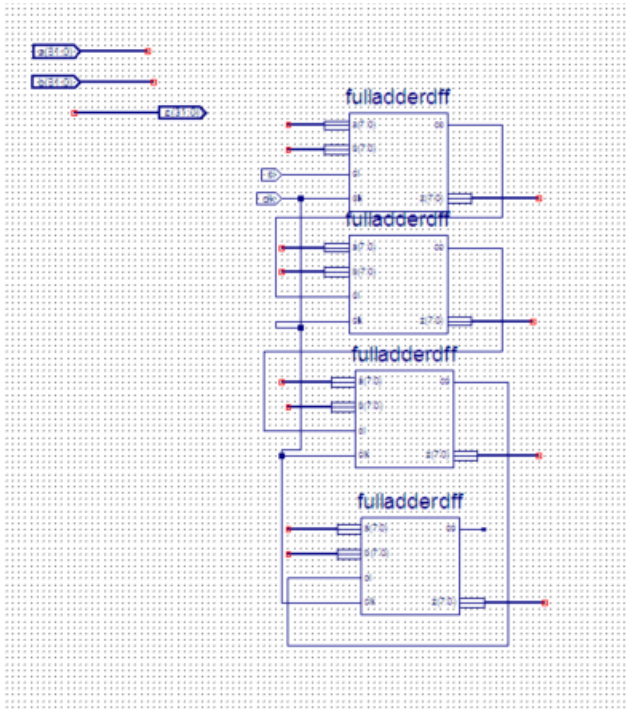

Testbench:

 


Simulation result:

 


2. Extending Adder into 32-bit ALU

Mux for ALU's sel


Schemaitic:

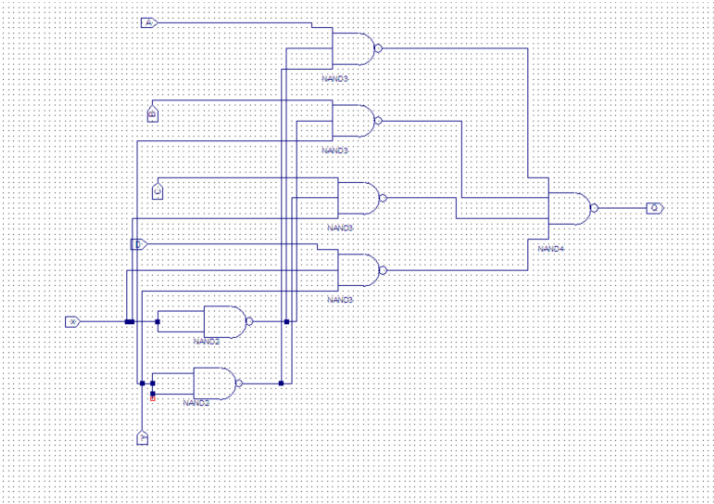

Testbench:

 


Simulation result:

 


5 input mux for sel


Schematic:

 


Simulation result:

 

AND function

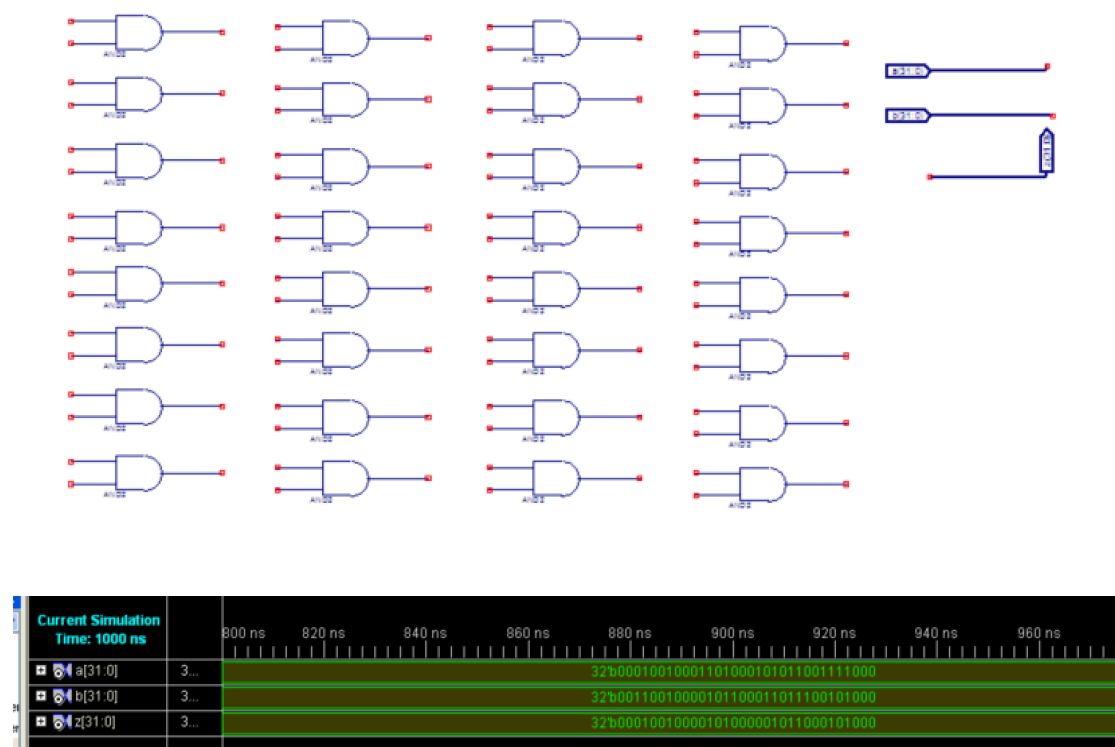


OR function

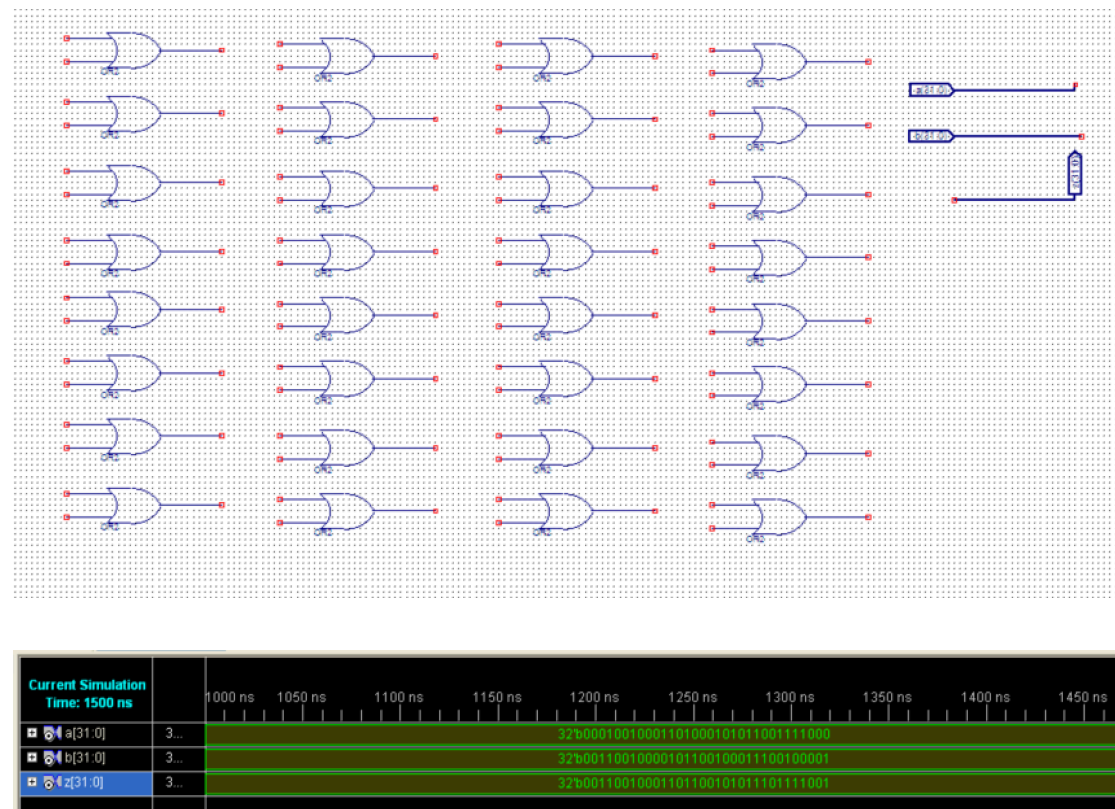


Subtractor


Schematic:

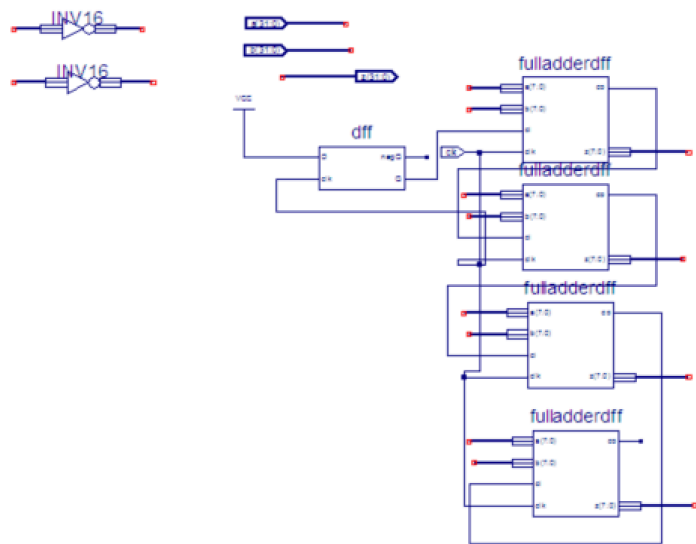

Testbench:

 


Simulation result:

 


ALU


Schematic:

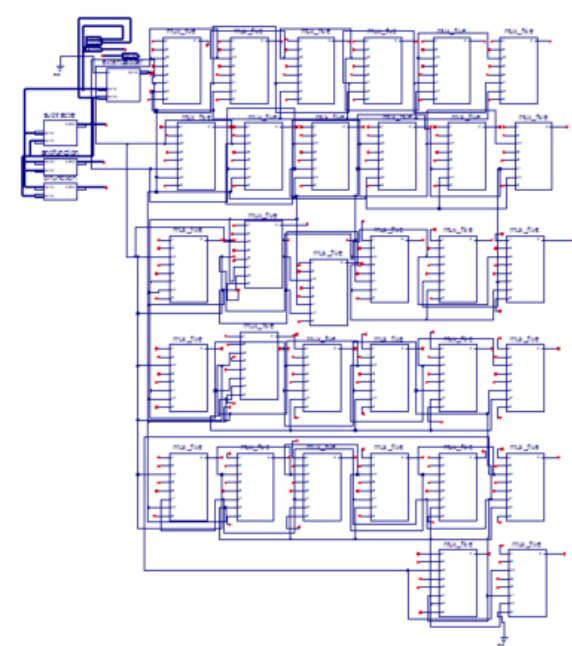


Add: sel=0

 


Sub: sel=1

 


And: sel=2

 

Or: sel=3

 

Shift right: sel=4

 

Log file of the mapper:

```
mapped into FPGA logic resources. It can also be used to analyze
preliminary, logic-level (pre-route) timing with one of the Xilinx static
timing analysis tools (TRCE or Timing Analyzer).

Design Summary
-----

Design Summary:
Number of errors:      1
Number of warnings:    0
Logic Utilization:
  Number of 4 input LUTs:      219 out of 1,536  14%
Logic Distribution:
  Number of occupied Slices:    114 out of 768  14%
  Number of Slices containing only related logic:  114 out of 114  100%
  Number of Slices containing unrelated logic:      0 out of 114   0%
  *See NOTES below for an explanation of the effects of unrelated logic
Total Number of 4 input LUTs:    219 out of 1,536  14%
  Number of bonded IOBs:        99 out of 98  101% (OVERMAPPED)

Peak Memory Usage: 130 MB
Total REAL time to MAP completion: 1 secs
Total CPU time to MAP completion: 1 secs


NOTES:

  Related logic is defined as being logic that shares connectivity - e.g. two
  LUTs are "related" if they share common inputs. When assembling slices,
  we attempt to place as much related logic as possible in a single slice.
```

Total LUTs = 219

Number of occupied Slices: 114

 Error: number of bonded IOBs 99 out of 98 101% (overmapped)




3. Verilog equivalent of 32-bit ALU Verilog


Verilog:

```
module ALUverilog(  
    input [31:0] x,  
    input [31:0] y,  
    input [2:0] sel,  
    output reg [31:0] z  
);  
  
always @(*) begin  
    case (sel)  
        3'd0: z = x+y;  
        3'd1: z = x-y;  
        3'd2: z = x&y;  
        3'd3: z = x|y;  
        3'd4: z = x>>1;  
        default: z = 32'd0;  
    endcase  
end  
  
endmodule
```


Add sel=0

 


Sub sel=1

 


And sel=2

 

Or sel=3

 

Shift right sel=4

 

Log file of the mapper:

fulladder Project Status [01/24/2025 - 17:53:37]					
Project File:	fulladder.isc	Current State:	Mapped		
Module Name:	ALUverilog	• Errors:	X 1 Error		
Target Device:	xc2s50e-6tq144	• Warnings:	1 Warning		
Product Version:	ISE 10.1 - Foundation Simulator	• Routing Results:			
Design Goal:	Balanced	• Timing Constraints:			
Design Strategy:	Xilinx Default (unlocked)	• Final Timing Score:			
fulladder Partition Summary					
No partition information was found.					
Device Utilization Summary					
Logic Utilization	Used	Available	Utilization	Note(s)	
Number of 4 input LUTs	97	1,536	6%		
Logic Distribution					
Number of occupied Slices	49	768	6%		
Number of Slices containing only related logic	49	49	100%		
Number of Slices containing unrelated logic	0	49	0%		
Total Number of 4 input LUTs	97	1,536	6%		
Number of bonded IOBs	99	98	101%	OVERMAPPE	
Detailed Reports					
Report Name	Status	Generated	Errors	Warnings	Infos
Synthesis Report	Current	Fri Jan 24 17:53:31 2025	0	1 Warning	1 Info
Translation Report	Current	Fri Jan 24 17:53:34 2025	0	0	0
Map Report	Current	Fri Jan 24 17:53:37 2025	X 1 Error	0	1 Info
Place and Route Report					
Static Timing Report					
Bitgen Report					
Date Generated: 01/24/2025 - 17:53:37					

Total LUTs = 97

Number of occupied Slices: 49

Brief comment on the number of gates as compared to the schematic version

1. Separate Paths for ADD and SUB

In a typical Verilog or RTL ALU, addition and subtraction can be implemented using one single 32-bit adder, combined with a 2's complement approach. This only requires one arithmetic circuit.

In a schematic-based design, I create a separate 32-bit adder for ADD and another 32-bit subtractor for SUB, the synthesis tool will see two distinct circuits and will not automatically merge them. Thus, more LUTs will be needed.

2. Multiple 5-to-1 MUX Instances (Multiplied by 32 Bits)

I use 32 instances of a 5-to-1 multiplexer to handle multiple ALU operations. Each 1-bit 5-to-1 MUX is constructed from multiple smaller logic gates or 2-input MUXes, so get a lot of replicated logic.

In contrast, when written in Verilog, the synthesis tool can generate an efficient LUT-based multiplexer or share logic to reduce resource usage.